

# ENGR3426: Miniproject 2

Jacob Smilg

September 26th 2023

## 1 Schematic Capture and Simulation

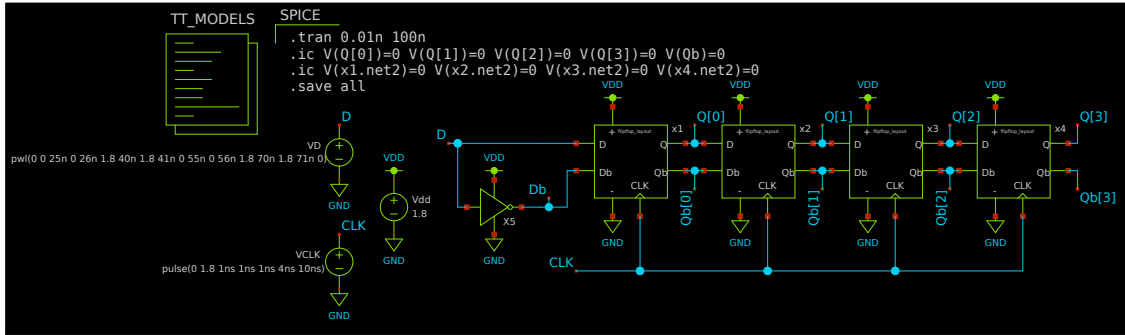


Figure 1: Schematic of my four-bit shift register simulation test harness created in Xschem.

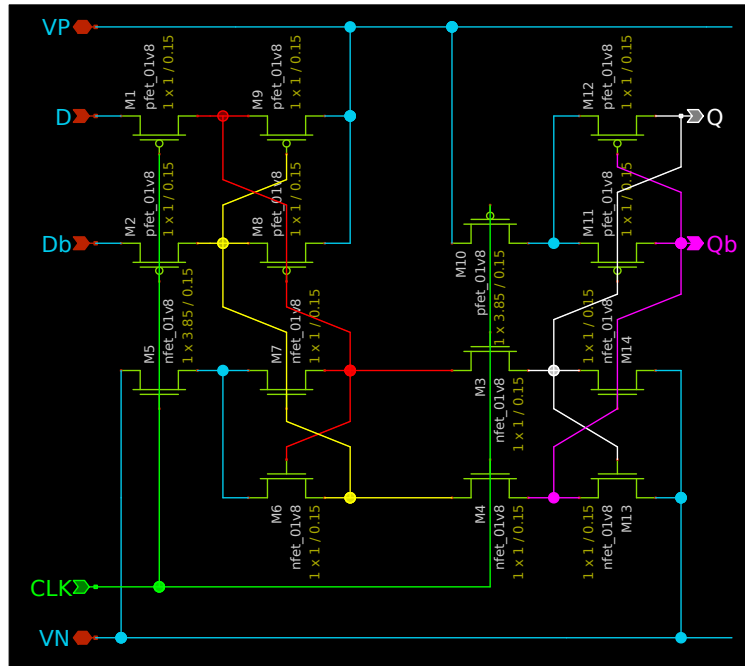


Figure 2: Layout-driven schematic of my D flip-flop created in Xschem. The dimensions of M5 and M10 are altered to account for the non-ratio-less-ness of the CSRL design.

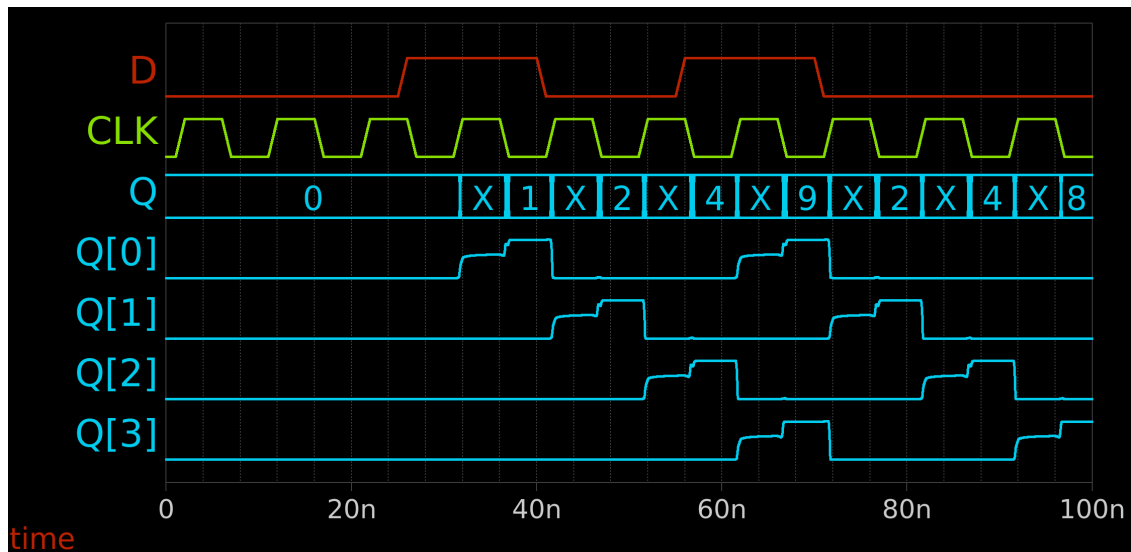


Figure 3: A plot of the output of the simulation of Figure 1. The shift register behaves as expected; the state of D propagates through the flip-flops on each rising edge of CLK.

## 2 Layout Design

 


Figure 4: A screenshot of the top-level layout of my four-bit shift register. The overall width of the shift register is 14.750 microns, and the height is 11.750 microns.

 


Figure 5: A screenshot of the cell layout of my D flip-flop. The clock signal and power and ground rails are routed horizontally in a metal layer, and the input enters the cell on the left and propagates to the right.



### 3 Layout Versus Schematic

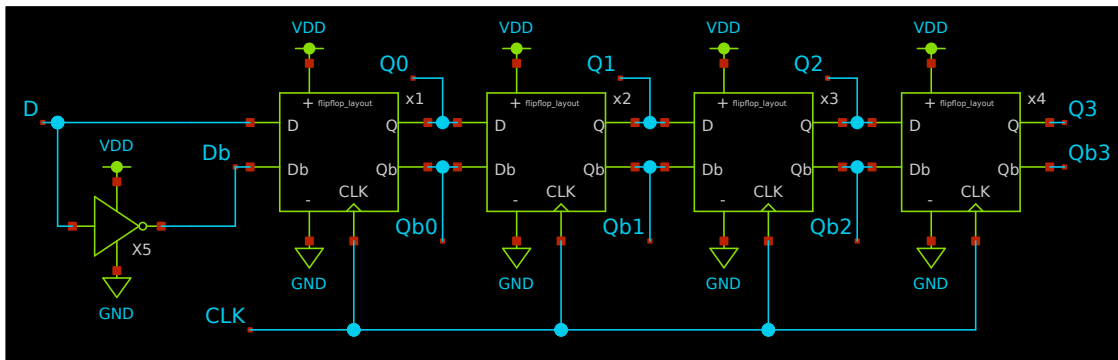


Figure 6: Schematic of my shift register separated from the simulation test harness for LVS.

#### 3.1 LVS Output Log

The following is the contents of the file `mp2/comp.out` obtained from running the netgen LVS program comparing `mp2/layout/shiftreg.spice` (Magic netlist) and `mp2/simulation/shiftreg.spice` (Xschem netlist). It shows that the layout and schematic match.

Circuit 1 cell sky130\_fd\_pr\_\_nfet\_01v8 and Circuit 2 cell sky130\_fd\_pr\_\_nfet\_01v8 are black boxes.

Equate elements: no current cell.

Device classes sky130\_fd\_pr\_\_nfet\_01v8 and sky130\_fd\_pr\_\_nfet\_01v8 are equivalent.

Circuit 1 cell sky130\_fd\_pr\_\_pfet\_01v8 and Circuit 2 cell sky130\_fd\_pr\_\_pfet\_01v8 are black boxes.

Equate elements: no current cell.

Device classes sky130\_fd\_pr\_\_pfet\_01v8 and sky130\_fd\_pr\_\_pfet\_01v8 are equivalent.

Subcircuit summary:

Circuit 1: inverter

Circuit 2: inverter

sky130\_fd\_pr\_\_nfet\_01v8 (1)

sky130\_fd\_pr\_\_nfet\_01v8 (1)

sky130\_fd\_pr\_\_pfet\_01v8 (1)

sky130\_fd\_pr\_\_pfet\_01v8 (1)

Number of devices: 2

Number of devices: 2

Number of nets: 4

Number of nets: 4

Netlists match uniquely.

Subcircuit pins:

Circuit 1: inverter

Circuit 2: inverter

Y

Y

A

A

VN

VN

VP

VP

Cell pin lists are equivalent.

Device classes inverter and inverter are equivalent.

Flattening unmatched subcell flipflop\_layout in circuit  
simulation/shiftreg.spice (0)(4 instances)

Flattening unmatched subcell flipflop in circuit layout/shiftreg.spice (1)(4 instances)

Subcircuit summary:

Circuit 1: simulation/shiftreg.spice

Circuit 2: layout/shiftreg.spice

inverter (1)

sky130\_fd\_pr\_\_pfet\_01v8 (28)

sky130\_fd\_pr\_\_nfet\_01v8 (28)

Number of devices: 57

Number of nets: 29

inverter (1)

sky130\_fd\_pr\_\_pfet\_01v8 (28)

sky130\_fd\_pr\_\_nfet\_01v8 (28)

Number of devices: 57

Number of nets: 29

Netlists match uniquely.

Cells have no pins; pin matching not needed.

Device classes simulation/shiftreg.spice and layout/shiftreg.spice are equivalent.

Final result: Circuits match uniquely.

.

## 4 Design Files

All of the files for this miniproject can be found at <https://github.com/smilg/madvlsi-fa23/tree/main/mp2>.